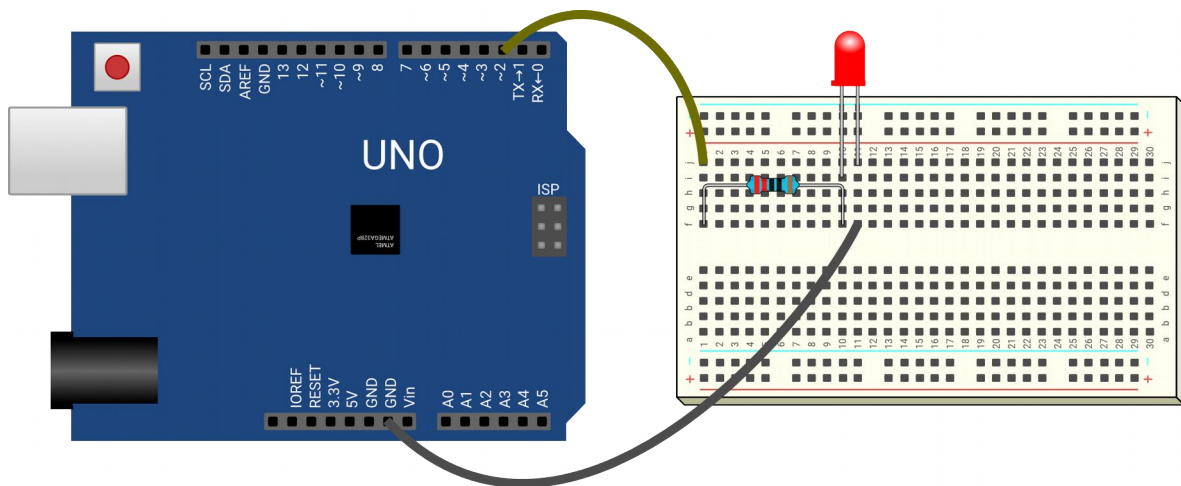


Arduino-project 001 – Blinking LED

The circuit

A very good project to start with if you're new to **Arduino** is to get a **LED** to blink. The first you need to do is connect it physically to the **Arduino board**. Do this according to the schematics below. Please note that the **LED** only works in one direction. The long leg connects to plus (the resistor) and the short leg connects to minus (GND). A **LED** may never be connected directly to a battery or other power source without a suitable **resistor** or other protection. In this instance we're using a **resistor** of 220 ohm (red-red-black-black) which is a good compromise for most **LEDs** connected to 5 volts. White and blue **LEDs** may need a smaller **resistor**, say 100 ohm, in order to shine at full power, but will work with 220 ohm.



Description

Copy the code below to **the Arduino development environment**, compile and upload to the Arduino board. When the board is powered the processor will first run `setup()`. The only thing `setup()` does is telling the processor that we want connection 2 to be an output. All digital connections on the Arduino board are set to be inputs at startup.

After this the `loop()` function takes over. This function will be called over and over again infinitely until the power to the board is removed or you push the reset-button. In `loop()` we first turn on the LED by setting connection 2 to high (5 Volts). Then we wait for half a second (500 ms). Then we turn the LED off by writing a zero on connection 2 and then we wait half a second again. After this the program ends, but as previously noted the `loop()` function will automatically be called again meaning that the program starts all over again, and so the **LED** will flash once per second.